



7.2.9 Conductors



30 minutes



32 marks

Q1. A set of Christmas tree lights is made from twenty identical lamps connected in series.



(a) Each lamp is designed to take a current of 0.25 A. The set plugs directly into the 230 V mains electricity supply.

(i) Write down the equation that links current, potential difference and resistance.

.....
.....

(1)

(ii) Calculate the resistance of **one** of the lamps. Show clearly how you work out your final answer and give the unit.

.....
.....
.....
.....

Resistance =

(4)

(iii) What is the total resistance of the set of lights?

.....
.....

Total resistance =

(1)

- (b) How does the resistance of a filament lamp change as the temperature of the filament changes?

.....


.....

.....

.....

(1)
(Total 7 marks)

Q2. A circuit diagram is shown below.

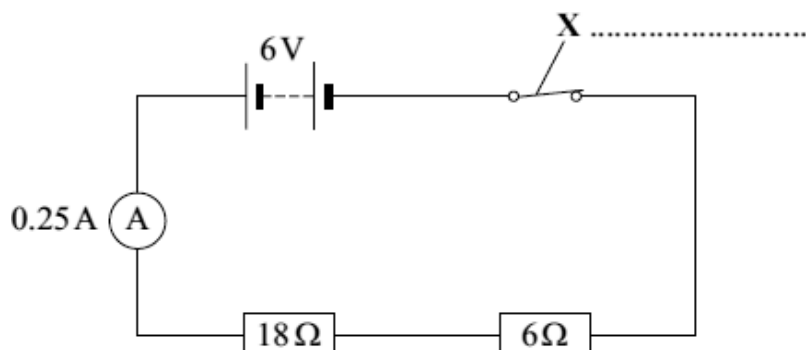

- (a) Use a word from the box to label component **X**.

fuse	switch	thermistor
-------------	---------------	-------------------

(1)

- (b) Calculate the total resistance of the two resistors in the circuit.

.....

Total resistance = Ω

(1)

- (c) The reading on the ammeter is 0.25 A.

The current through the 6 Ω resistor will be:

bigger than 0.25 A **equal to 0.25 A** **smaller than 0.25 A**

Draw a ring around your answer

(1)

- (d) The 6 V battery is made by correctly joining several 1.5 V cells in series.

Calculate the number of cells needed to make the battery.


.....

Number of cells =

(1)

(Total 4 marks)

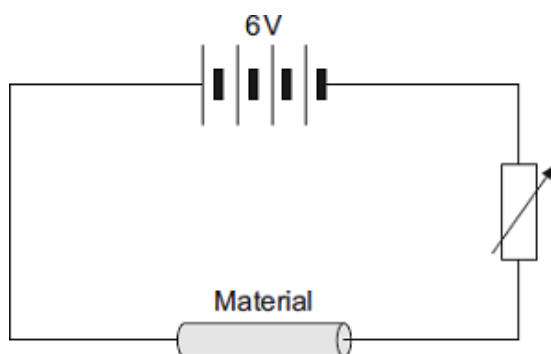- Q3.** (a) The diagram shows the circuit used to investigate the resistance of a sample of a material.
The diagram is not complete; the ammeter and voltmeter are missing.



- (i) Draw the symbols for the ammeter and voltmeter on the diagram in the correct places.

(2)

- (ii) How can the current through the material be changed?


.....

.....

(1)

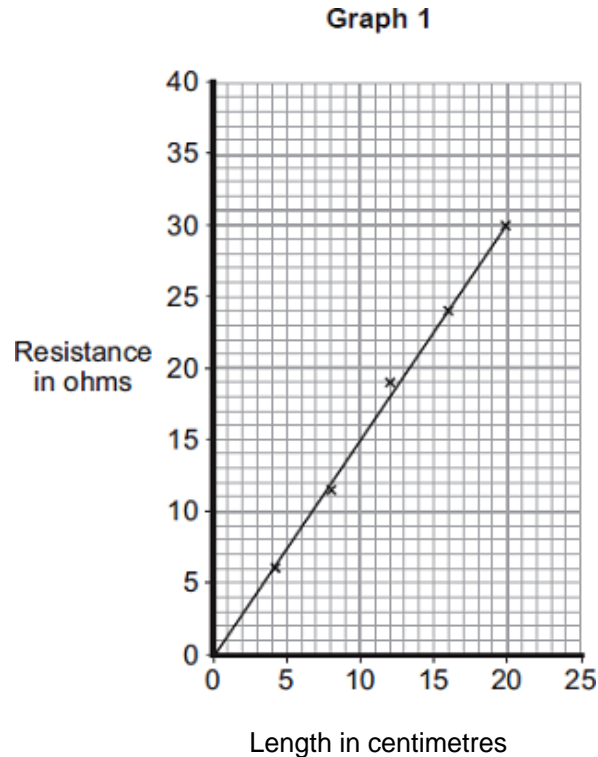- (b) The material, called conducting putty, is rolled into cylinders of different lengths but with equal thickness.

Graph 1 shows how the resistance changes with length.



- (i) The current through a 25 cm length of conducting putty was 0.15 A.

Use **Graph 1** to find the resistance of a 25 cm length of conducting putty.

Resistance = ohms

(1)

- (ii) Use your answer to **(b) (i)** and the equation in the box to calculate the potential difference across a 25 cm length of conducting putty.

potential difference = current x resistance

Show clearly how you work out your answer.

.....


.....

.....

Potential difference = volts

(2)

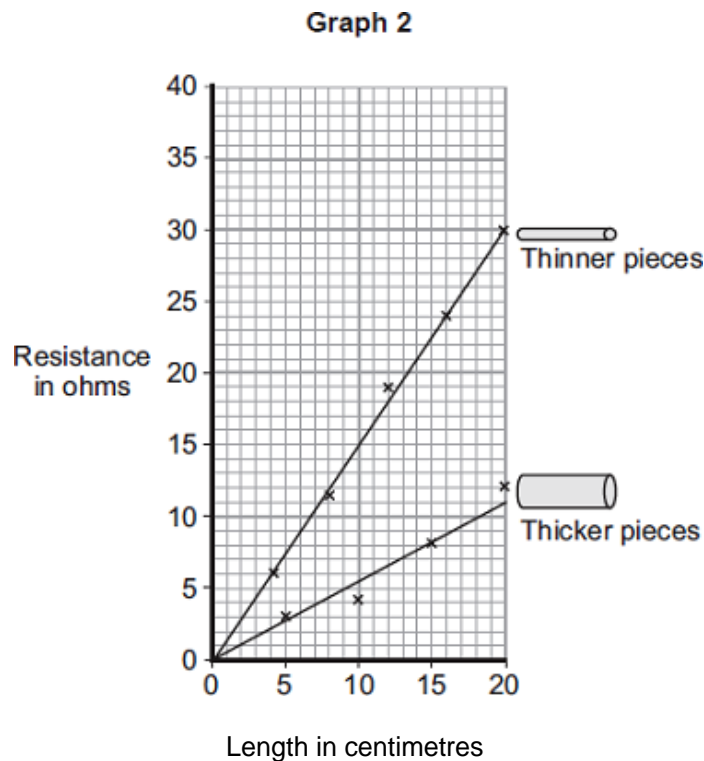- (c) A second set of data was obtained using thicker pieces of conducting putty. Both sets of results are shown in **Graph 2**.



- (i) What is the relationship between the resistance and the thickness of the conducting putty?

.....

(1)

- (ii) Name **one** error that may have reduced the accuracy of the results.

.....

(1)

- (iii) How could the reliability of the data have been improved?


.....

(1)

(Total 9 marks)
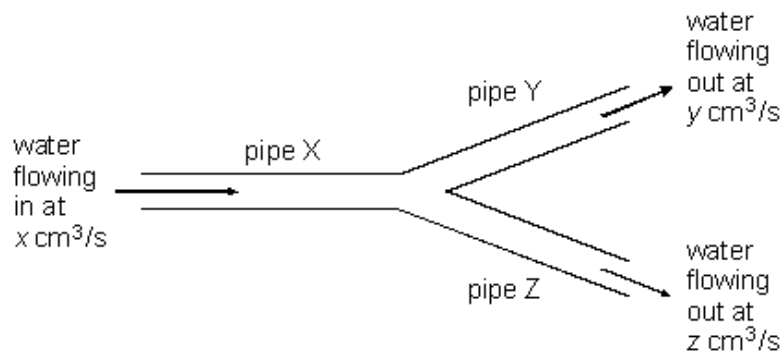
##

The flow of water through tubes can be used as a model to explain some of the rules about electrical circuits.




The diagram shows a junction in a water pipe.
The rate of flow in the pipes is measured in cm^3/s .

- (a) What is the relationship between the rate of flow in the three pipes, **X**, **Y** and **Z**?

.....

1 mark

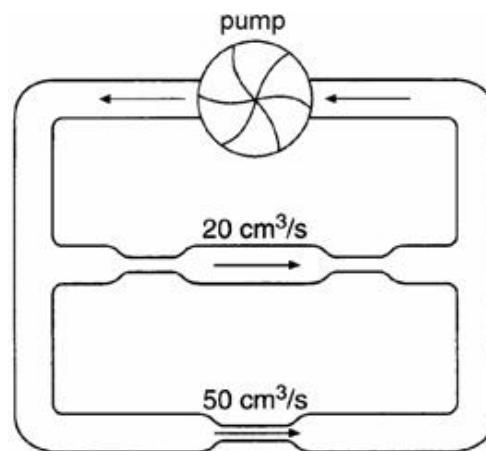- (b) The diagram below shows a 'water circuit', in which water is forced round by a pump. The rates of flow at two places are written on the diagram.



- (i) At what rate is water flowing:

into the pump? cm^3/s

out of the pump? cm^3/s

1 mark

- (ii) The 'water circuit' can be used as a model of an electrical circuit.
Each part of the 'water circuit' is equivalent to a part of an electrical circuit.

What is the electrical equivalent of the water?

.....

1 mark

A family, who did not understand electricity very well, always made sure there was a bulb in each of the light fittings in their house. They were afraid that electricity would escape from an empty light socket when the switch was turned on.

- (c) Explain why electricity does **not** escape from an empty light socket.


.....

.....

.....

1 mark
Maximum 4 marks

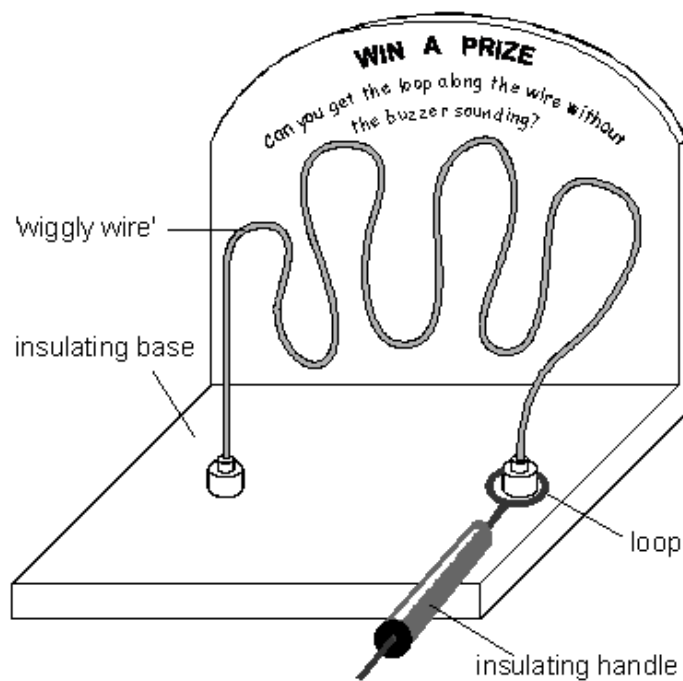- Q5.** Anne makes an electrical 'wiggly wire' game for a fête. To win a prize, the loop must not touch the 'wiggly wire'.



- (a) The loop is made of a conducting material. The handle is made of an insulating material.

Give the name of **one** material which could be used to make:

- (i) the loop;

.....


1 mark

- (ii) the insulation handle.

.....

1 mark

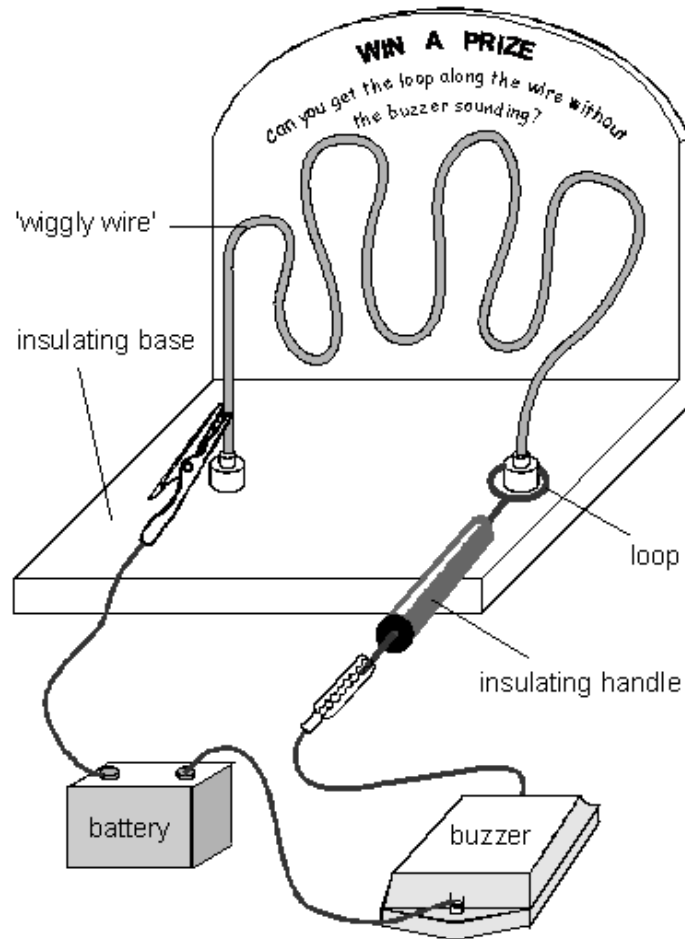- (b) The loop and the 'wiggly wire' are connected to a battery and a buzzer.



The buzzer only makes a noise when the loop touches the 'wiggly wire'. Explain why.

.....

.....

1 mark

- (c) Later, Anne paints the 'wiggly wire', but then the game does **not** work. Suggest why the game does **not** work with a painted wire.


.....

.....

1 mark
Maximum 4 marks

Q6.

(a) Max built **circuit 1** as shown below.

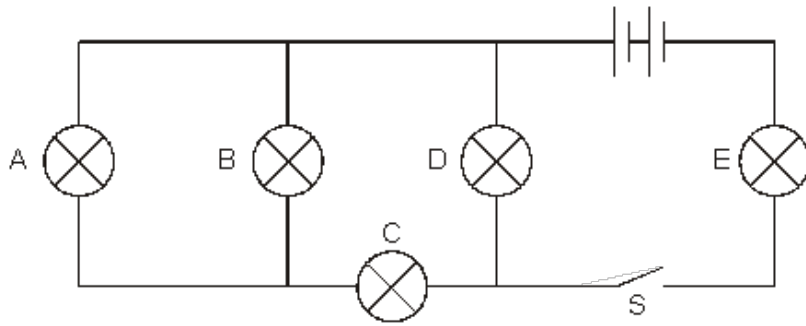

circuit 1

He closed the switch, S, and all the bulbs came on.
One of the bulbs then broke and **all** the bulbs went off.


Which bulb must have broken?
Give the letter.

.....

1 mark

(b) Max built **circuit 2** as shown below.

He connected a plastic comb and a metal key in different parts of the circuit.

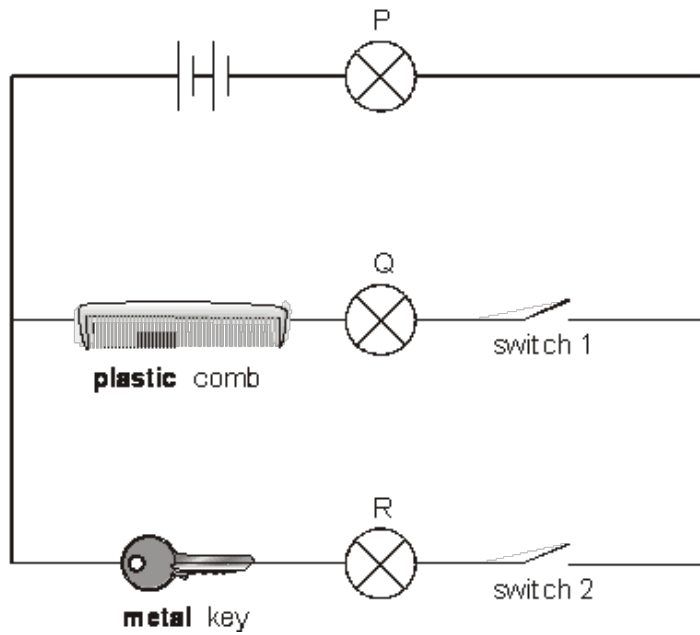


circuit 2

Look carefully at **circuit 2**.
 Complete the table below to show which bulbs in circuit 2 will be on or off when different switches are open or closed.
 Write **on** or **off** in the boxes below.

switch 1	switch 2	bulb P	bulb Q	bulb R
open	open	off	off	off
open	closed			
closed	open			

2 marks

(c) Max built **circuit 3** using a battery, two bulbs and three ammeters.

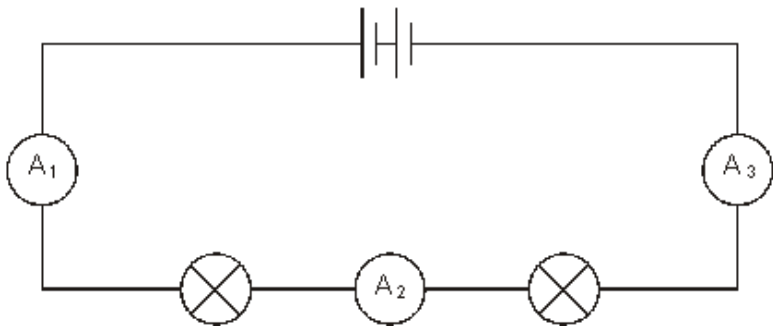

circuit 3

The current reading on ammeter A_1 was 0.8 amps.
 What would be the reading on ammeters A_2 and A_3 ?
 Place **one** tick in the table by the correct pair of readings.

reading on ammeter A_2 (amps)	reading on ammeter A_3 (amps)	correct pair of readings
0.8	0.8	
0.8	0.4	
0.4	0.8	
0.4	0.4	

1 mark
 maximum 4 marks

